

Assignment 7: Applied Programming Lab

Aman Singhal, EP17B002

7 April 2020

1 Abstract

In this assignment, the focus will be on two powerful capabilities of Python:

- 1) Symbolic Algebra
- 2) Analysis of Circuits using Laplace Transforms

2 My Code

```
1 from sympy import symbols, lambdify, Matrix, numer, denom
2 import numpy as np
3 import matplotlib.pyplot as plt
4 import scipy.signal as sp
5
6 ww = np.logspace(-1, 10, 1000)
7 ss = 1j*ww
8 s = symbols('s')
9
10 def lowpass(R1,R2,C1,C2,G,Vi):
11     A=Matrix([[0,0,1,-1/G],
12               [-1/(1+s*R2*C2),1,0,0],
13               [0,-G,G,1],
14               [-1/R1-1/R2-s*C1,1/R2,0,s*C1]])
15     b=Matrix([0,0,0,Vi/R1])
16     V=A.inv()*b
17     return (A,b,V)
18
19 def highpass(R1,R2,C1,C2,G,Vi):
20     s = symbols('s')
21     A = Matrix([[0,0,1,-1/G],
22                 [-s*R2*C2/(1+s*R2*C2),1,0,0],
23                 [0,-G,G,1],
24                 [-1/R1-s*C2-s*C1,s*C2,0,1/R1]])
25     b = Matrix([0,0,0,-Vi*s*C1])
26     V = A.inv()*b
27     return (A,b,V)
28
29 def inp(f1,f2,t):
30     return (np.sin(2*np.pi*f1*t) * np.cos(2*np.pi*f2*t))*np.heaviside(t,2)
31
32 def damped_sinusoid(f,a,t):
33     return np.cos(2*np.pi*f*t)* np.exp(-a*t)*np.heaviside(t,2)
```

```

34
35
36 #pdf
37 A_lp,b_lp,V_lp=lowpass(10000,10000,1e-9,1e-9,1.586,1)
38 Vo_lp = V_lp[3]
39 hf_lp = lambdify(s,Vo_lp,'numpy')
40 bode_output_lp = hf_lp(ss)
41 plt.loglog(ww,abs(bode_output_lp),lw=2)
42 plt.title("bode plot of lowpass filter")
43 plt.xlabel('frequency')
44 plt.ylabel('H(jw)')
45 plt.grid(True)
46 plt.show()
47
48 numerator_lp = [float( numer(Vo_lp.simplify()).coeff(s, 2)),float( numer(
    Vo_lp.simplify()).coeff(s, 1)),float( numer(Vo_lp.simplify()).coeff(s,
    0))]
49 denominator_lp = [float( denom(Vo_lp.simplify()).coeff(s, 2)), float( denom(
    Vo_lp.simplify()).coeff(s, 1)), float( denom(Vo_lp.simplify()).coeff(s,
    0))]
50
51
52 #1
53 v, t = sp.step([numerator_lp, denominator_lp], None, np.arange(0, 1e-3, 1e
    -6))
54 plt.plot(v, t)
55 plt.title("Step response of lowpass filter")
56 plt.grid(True)
57 plt.xlabel('t')
58 plt.ylabel('Vo')
59 plt.show()
60
61
62 #2
63 t1 = np.arange(0,1e-2,1e-6)
64 x,y,svec = sp.lsim([numerator_lp, denominator_lp], inp(1e3,1e6,t1), t1)
65 plt.plot(x, y)
66 plt.grid(True)
67 plt.title("response of low pass filter for sin(2e3*pi*t)+cos(2e6*pi*t) as
    input")
68 plt.xlabel('t')
69 plt.ylabel('Vo')
70 plt.show()
71
72
73 #3
74 A_hp,b_hp,V_hp=highpass(10000,10000,1e-9,1e-9,1.586,1)
75 Vo_hp = V_hp[3]
76 hf_hp = lambdify(s,Vo_hp,'numpy')
77 bode_output_hp = hf_hp(ss)
78 plt.loglog(ww,abs(bode_output_hp),lw=2)
79 plt.title("bpde plot of highpass filter")
80 plt.xlabel('frequency')
81 plt.ylabel('H(jw)')
82 plt.grid(True)
83 plt.show()
84
85 numerator_hp = [float( numer(Vo_hp.simplify()).coeff(s, 2)),float( numer(
    Vo_hp.simplify()).coeff(s, 1)),float( numer(Vo_hp.simplify()).coeff(s,

```

```

0))]
86 denominator_hp = [float(denom(Vo_hp.simplify()).coeff(s, 2)), float(denom(
    Vo_hp.simplify()).coeff(s, 1)), float(denom(Vo_hp.simplify()).coeff(s,
    0))]
87
88
89 #4a(low frequency)
90 t2 = np.arange(1e-5, 5e-4, 1e-7)
91 x,y,svec = sp.lsim([numerator_hp, denominator_hp], damped_sinusoid(1e4,1e6,
    t2), t2)
92 plt.plot(x, y)
93 plt.grid(True)
94 plt.title("response of high pass filter for cos(2e4*pi*t)*exp(-1e6*t) as
    input")
95 plt.xlabel('t')
96 plt.ylabel('Vo')
97 plt.show()
98
99
100 #4b(high frequency)
101 t2 = np.arange(1e-9, 5e-7, 1e-9)
102 x,y,svec = sp.lsim([numerator_hp, denominator_hp], damped_sinusoid(1e7,1e6,
    t2), t2)
103 plt.plot(x, y)
104 plt.grid(True)
105 plt.title("response of high pass filter for cos(2e7*pi*t)*exp(-1e6*t) as
    input")
106 plt.xlabel('t')
107 plt.ylabel('Vo')
108 plt.show()
109
110
111
112 #5
113 A_hp,b_hp,V_hp=highpass(10000,10000,1e-9,1e-9,1.586,1/s)
114 Vo_hp = V_hp[3]
115 hf_hp = lambdify(s,Vo_hp,'numpy')
116 bode_output_hp = hf_hp(ss)
117 plt.loglog(w,abs(bode_output_hp),lw=2)
118 plt.title("replacing Vi from 1 to 1/s for high pass filter")
119 plt.xlabel('frequency')
120 plt.ylabel('H(jw)')
121 plt.grid(True)
122 plt.show()

```

3 Plots

3.1 Question 1

The transfer function of the first circuit represents a low pass filter. The bode plot of the transfer function is given by:

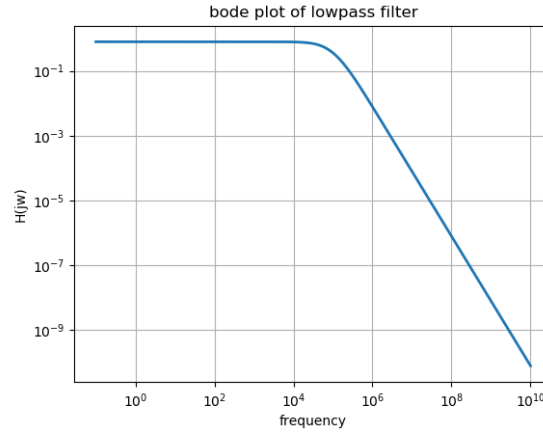


Figure 1

3.2 Question 2

If we give a step input to the first low pass circuit we get the following response:

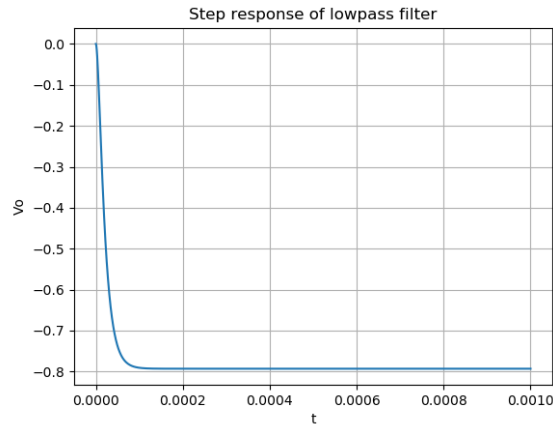


Figure 2

3.3 Question 3

Giving a superposition of a low and high frequency as an input to the low pass filter ie. $\sin(2e3*\pi*t)+\cos(2e6*\pi*t)$

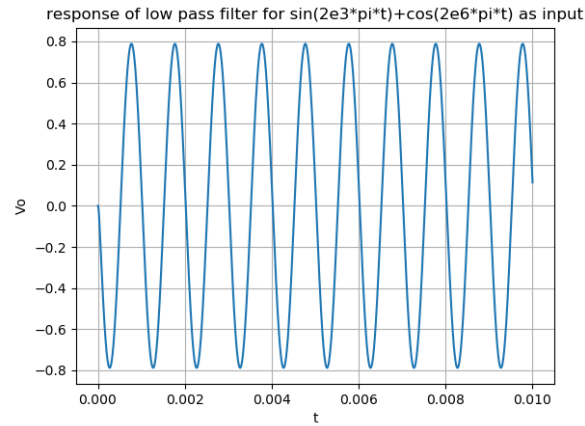


Figure 3

3.4 Question 4

The transfer function of the second circuit represents a high pass filter. The bode plot of the transfer function is given by:


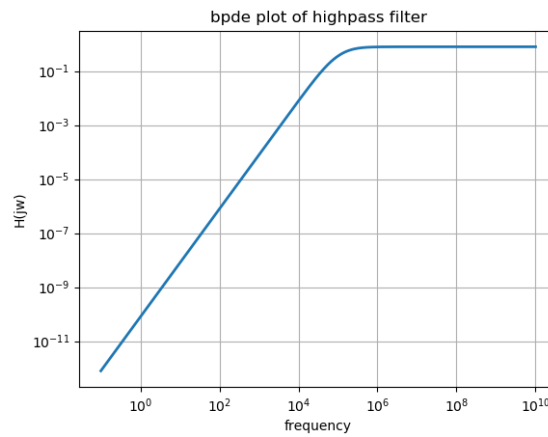
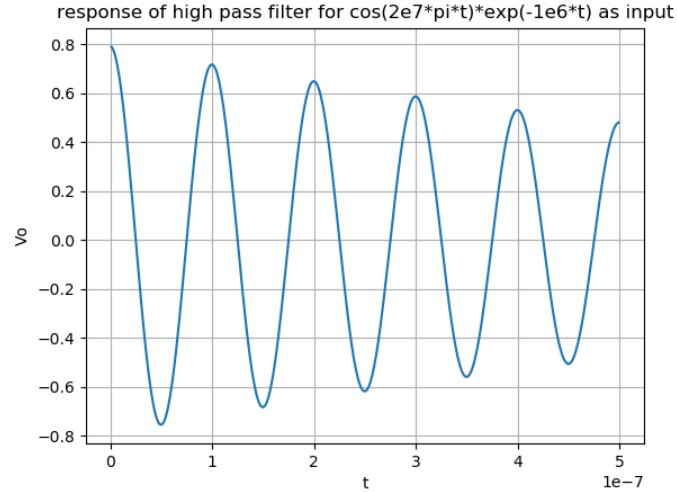


Figure 4

3.5 Question 5

Here I have given two different inputs to the high pass filter:

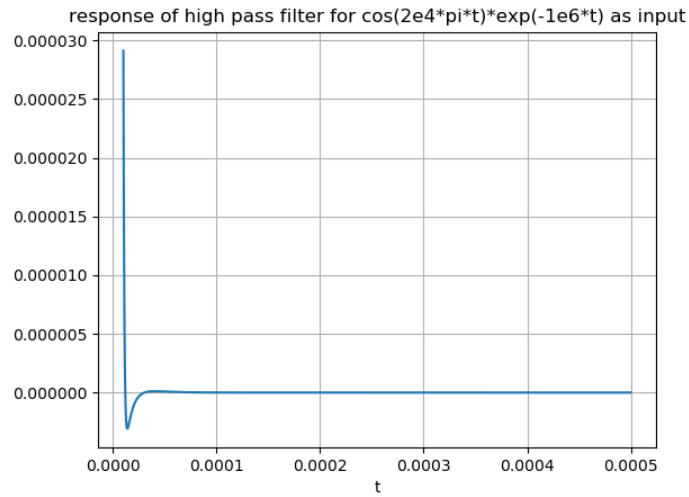- 1) low frequency light damping
- 2) high frequency light damping



3.6 Question 6

Response of the high pass filter circuit to a unit step function.

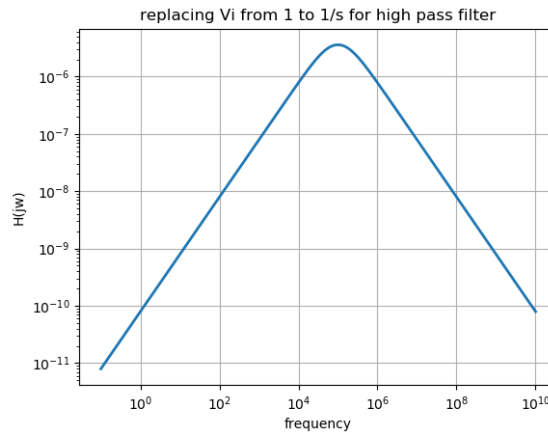


Figure 6

4 Conclusion

- 1) In question 2, the circuit is a low pass circuit so it allows dc to pass with some negative gain.
- 2) In question 3, the circuit being a low pass filter, we observe that the lower frequency passes with some gain but the higher frequency is blocked
- 3) In question 5 the circuit being a high pass filter, we observe that the higher frequency passes with some gain but the lower frequency is blocked
- 4) Step response of a high pass filter resembles a band pass filters response